

**1. Complete the following diagram to show the connection of an ammeter.**

**2. Complete the following diagram to show the connection of a voltmeter.**

**3. Complete the following diagram to show the connection of a wattmeter.**

**4. Complete the following diagram to show the connection of an ammeter, voltmeter and wattmeter, so that power factor can be calculated.**