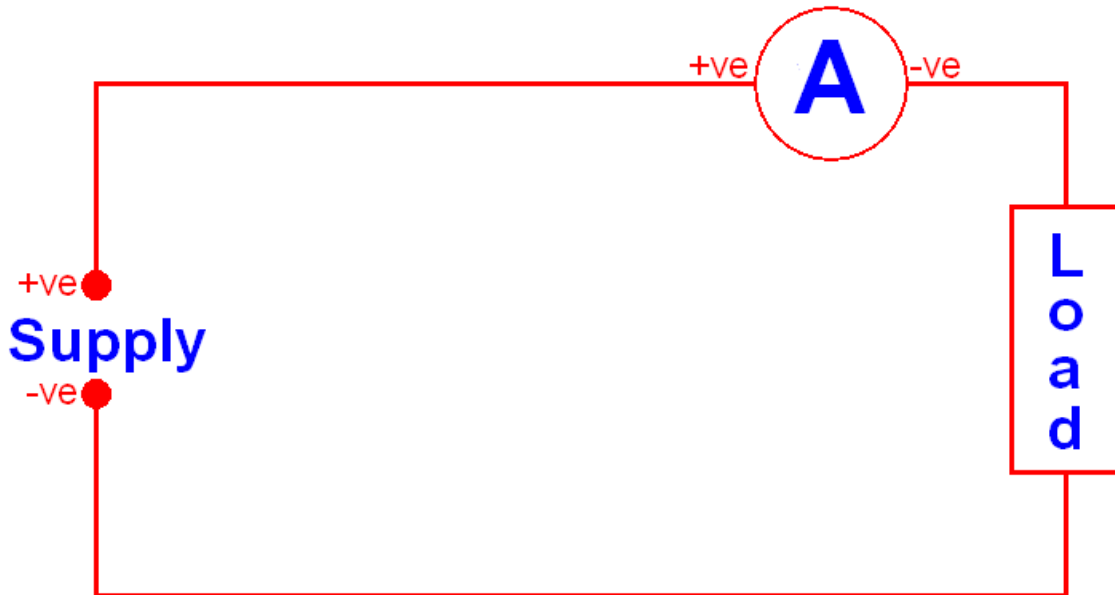

202: Principles of electrical science


Worksheet 8: Connection of meters

Answer guide


1. Complete the following diagram to show the connection of an ammeter.



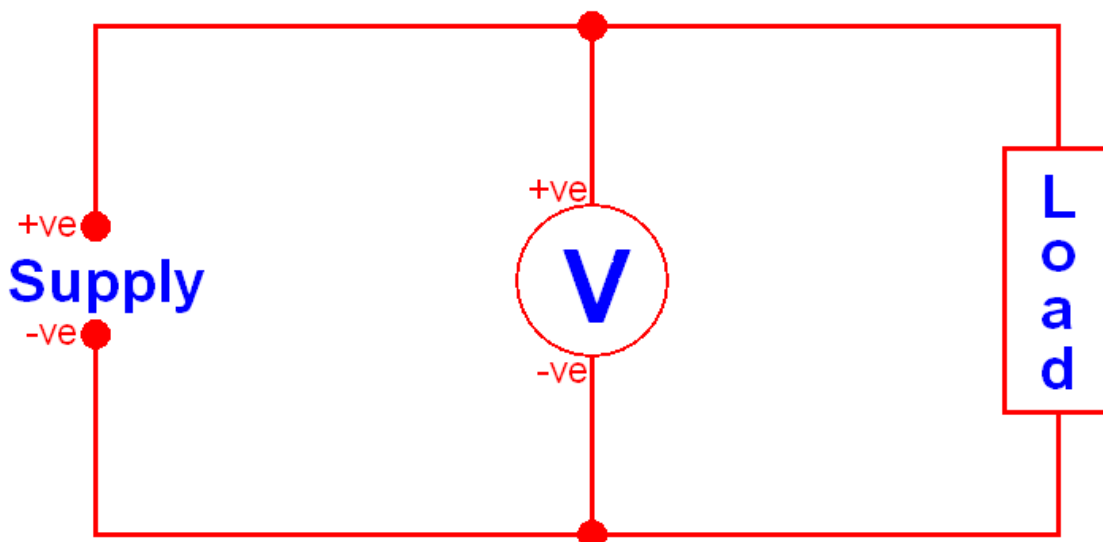2. Complete the following diagram to show the connection of a voltmeter.



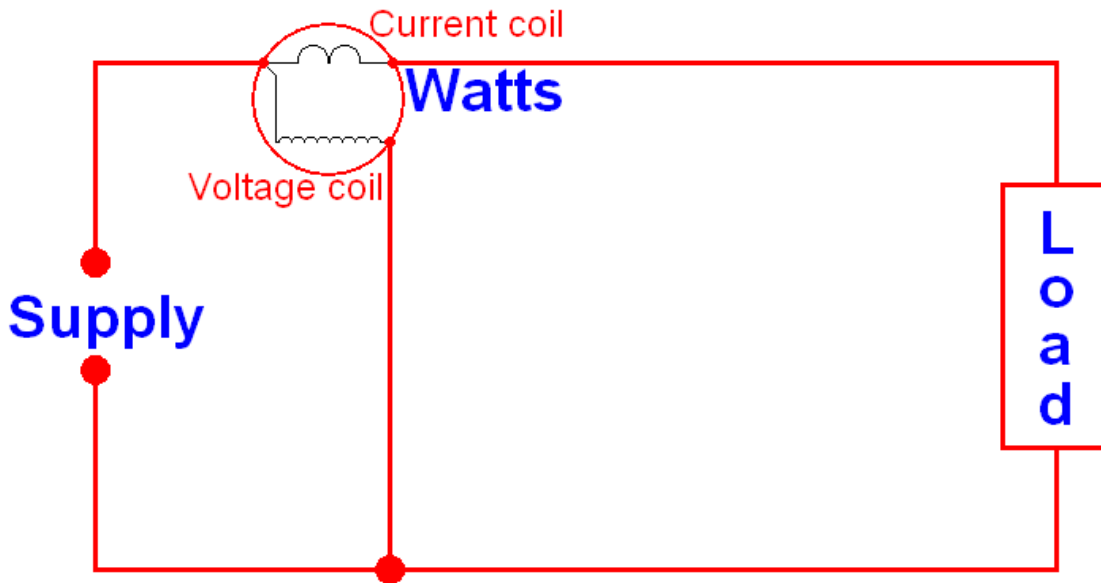3. Complete the following diagram to show the connection of a wattmeter.



4. Complete the following diagram to show the connection of an ammeter, voltmeter and wattmeter, so that power factor can be calculated.

